





An INPUT transformer is driven by the balanced line and is typically loaded by the input of an amplifier stage. Its primary must have a high impedance to the differential voltage between the lines and this requires more turns of smaller wire producing relatively higher resistance windings. The transformer must also suppress any response to the common-mode voltage. A Faraday shield, connected to ground, is used to prevent capacitive coupling of the common-mode voltage from primary to secondary. Placing this thin copper foil between windings also reduces magnetic coupling, resulting in increased "leakage inductance". To maintain impedance balance of the input line, the capacitance of the primary to the Faraday shield must be uniformly distributed across the winding. Because of its generally higher impedances and relatively high leakage inductance, *the secondary load on an input transformer must be carefully controlled*. The recommended load resistance and/or RC network must be used and load capacitance kept to a minimum. Generally, this means physically placing the input transformer as close as possible to the input amplifier stage. For example, the capacitance of 2 feet of shielded cable, about 100 pF, on the secondary of some input transformers will degrade bandwidth and transient response.
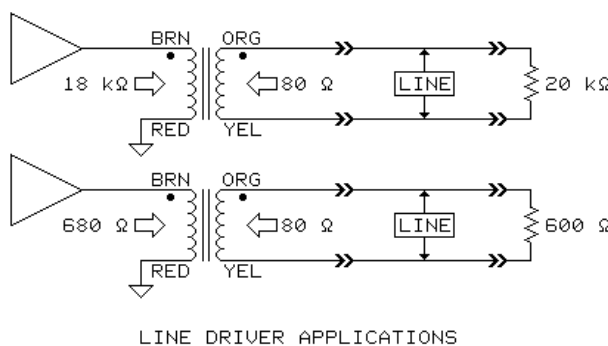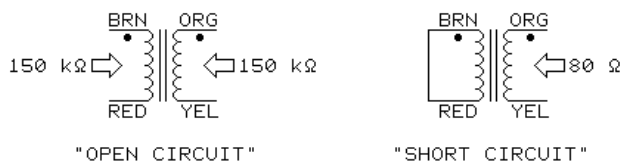
#### WHAT'S THE "IMPEDANCE" OF A TRANSFORMER ?

The "impedance" specification of audio transformers seems to confuse many engineers. Although they tend to produce optimum results when used with specified external impedances, *the transformer itself has no intrinsic impedance*. It simply reflects impedances, modified by the square of the turns ratio, from one winding to another. Keeping in mind that input and output power are equal, some simple application of Ohm's law will prove this.

The confusion probably stems from the fact that *transformers can simultaneously reflect two different impedances*. One is the impedance of the driving source, as seen from the secondary, and the other is the impedance of the load, as seen from the primary. An example of *output* transformer properties is shown below.




#### Jensen JT-11-DM 1:1 Output Transformer

The open circuit impedance, at 1 kHz, of either winding is about 150 kΩ. Since the DC resistance is about 40 Ω per winding, if the

primary is short circuited, the secondary impedance will be 80 Ω. If we place the transformer between an amplifier and a load, the amplifier will "see" the load through the transformer and the load will "see" the amplifier output impedance (generally tenths of an ohm for amplifiers with negative feedback) through the transformer. In our example, the amplifier would "look like" 80 Ω to the output line or load and the 600 Ω load would "look like" 680 Ω to the amplifier. If the load were 20 kΩ, it would "look like" slightly less than 20 kΩ because the open circuit transformer impedance is effectively in parallel with it. For most loads, this effect is negligible.

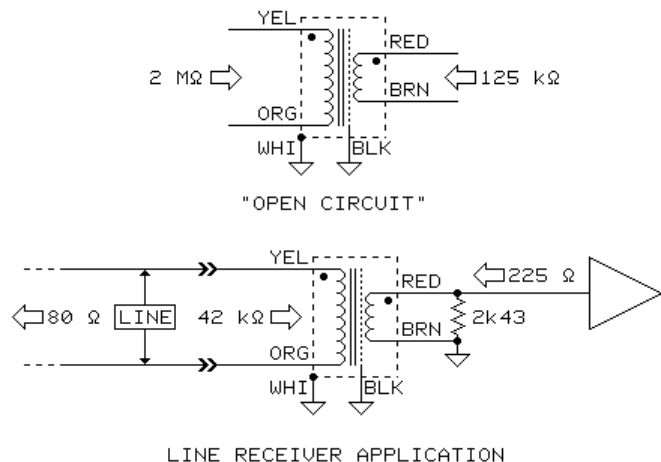An example of *input* transformer properties is shown below.



#### Jensen JT-10KB-D 4:1 Input Transformer

The open circuit impedance, at 1 kHz, of the primary is about 2 MΩ. Because this transformer has a 4:1 turns ratio, therefore 16:1 impedance ratio, the secondary open circuit impedance is about 125 kΩ. The DC resistances are about 2.5 kΩ for the primary and 92 Ω for the secondary. Since this is an input transformer, it must be used with the specified secondary load resistance of 2.43 kΩ for proper frequency and time domain responses. We can calculate that this load will "look like" about 42 kΩ at the primary, which certainly makes it suitable for a "bridging" input stage. To minimize the noise contribution of the amplifier stage, we need to know what the transformer secondary "looks like", impedance wise, to the amplifier. If we assume that the primary is driven from the line in our previous output transformer example with its 80 Ω source impedance, we can calculate that the secondary will "look like" about 225 Ω to the amplifier input.

#### REFERENCES:

B. Whitlock, "Balanced Lines in Audio - Fact, Fiction, and Transformers", Journal of the AES, Vol 43, No 6, June, 1995.

Copyright 1995, Jensen Transformers, Inc.

**Jensen Transformers, Inc.**  
7135 Hayvenhurst Avenue  
Van Nuys, California 91406

Tel (818) 374-5857 or (213) 876-0059  
Fax (818) 763-4574